

**CARMEL COLLEGE OF ARTS, SCIENCE & COMMERCE FOR WOMEN,
NUVEM - GOA.**

**SEMESTER END EXAMINATION, August 2020
B. Sc Semester: V old course PHYSICS (Paper I) -Electronics**

Total Marks: 30 Date: 04/08/2020 Duration: 2 Hours Total No of pages: 2

-
- Instructions:**
- 1) All questions are compulsory.
 - 2) Figures to the right indicate marks.
 - 3) Symbols have their usual meaning, unless otherwise stated.
 - 4) Use of log tables and non programmable calculators is allowed.

Q I. Answer any **five** of the following. **(5 x 2 marks = 10)**

- a) In case of op-amp what is meant by virtual ground? State any four characteristics of an ideal op-amp.
- b) Draw a functional circuit diagram of IC 555 timer. State the function of each basic block of the timer.
- c) For a transistor working as switch, what is meant by hard saturation and soft saturation.
- d) What is the working principle of current regulating diode (CRD)
- e) Draw the ideal voltage transfer curve of an op-amp. What is meant by comparator and window comparator?
- f) Convert the decimal number 36.43625 to binary and binary 10110 to BCD.
- g) State De Morgan's Law's laws for two inputs and verify the same by writing the truth table for two inputs.
- h) A truth table has output 0 for each of these input conditions: ABC = 001, 100 and 101. Write a POS expression for the output and draw a logical circuit diagram.

Q II. Answer any **four** of the following. **(4 x 5 marks = 20)**

- 1. a) Draw the circuit diagram of a Fixed Bias circuit. If this circuit is to work as a switch, write the expression for the minimum value of transistor h_{fe} and the value of the voltage across the collector.
- b) Draw the drain and transfer characteristics of N-channel JFET. Why is the input impedance of JFET large?
- 2. a) Explain how FET can be used as a Voltage Variable Resistor (VVR).
- b) With the help of a neat circuit and waveform diagram explain the working of a transistorized astable multivibrator. Write expression for the period of oscillations.

3. a) Draw the circuit diagram of an Integrator using op-amp. Sketch the nature of output waveform when a sine wave is applied at the input.
- b) Draw a functional circuit diagram of IC 555 when connected in monostable mode and write the expression for its pulse width.
4. Explain decimal to BCD encoder with a logical diagram.
5. Discuss 3 bit shift right register with logical diagram and waveforms.
6. Explain the working of a Mod 5 counter with logical diagram, input and output waveforms.

-----X-----