

Total marks: 60 Date: 28/11/2022 Duration: 2 Hours Total No of pages: 02

**Instructions:**

- 1) All questions are compulsory, however internal choice is available.
- 2) Figures to the right indicate maximum marks to the question.
- 3) Symbols have their usual meanings unless otherwise stated.
- 4) Draw neat diagram wherever necessary.
- 5) Use of non-programmable calculator is permitted.

**Q.1. Answer any Five of the following questions.**

**(2 x 5 = 10)**

- a) Explain the working of constant current source.
- b) State the principal of non-inductive resistance coil.
- c) State Kirchhoff's voltage law.
- d) Sketch the graph to show the resonance in a series LCR resonance circuit.
- e) State the application of Wheatstone A.C. Bridge.
- f) What is meant by a two-port network?
- g) List different kinds of losses in a transformers.

**Q.2. Answer any Five of the following questions.**


**(2 x 5 = 10)**

- a) What is meant by an ideal power source?
- b) Calculate the total inductance of the coils 1mH, 2mH and 3mH connected in parallel.
- c) State the principal based on which a transformer works.
- d) Capacitive reactance in D.C. circuit is infinite. Explain.
- e) Why there is no power factor or power factor is zero for a pure inductor or capacitor?
- f) Draw DeSauty's Capacitance Bridge and also write the balancing condition.
- g) State the significance of the time constant in a LR circuits.

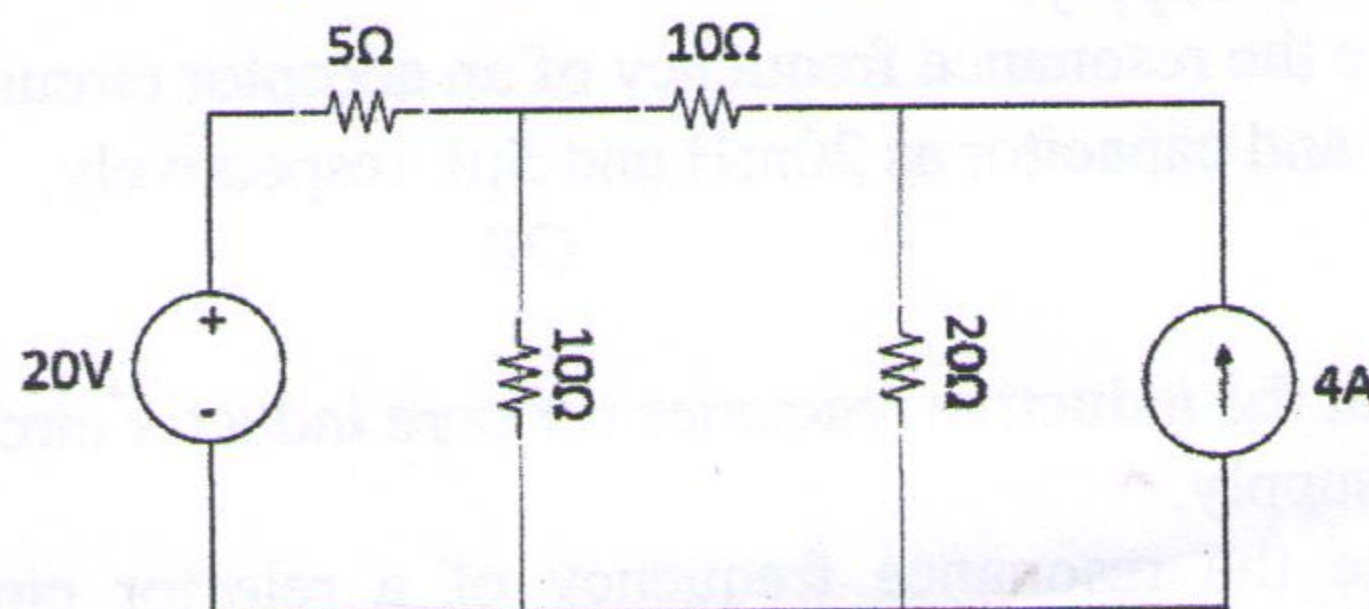**Q.3.(A)**

(p) State the limitations of the Superposition theorem. **(2)**

(q) Find the current flowing through  $20\Omega$  using the superposition theorem. **(3)**



**OR**

**Q.3.(A)**

(x) State Thevenin's Theorem. **(2)**

(y) Draw neat diagram of two coils of self-inductance  $L_1$  and  $L_2$  are connected in parallel and Derive the expression for the total inductance. **(3)**



**Q.3.(B)**

State Norton's Theorem and draw a Norton equivalent circuit to demonstrate the same. (5)

**Q.4.(A)**

(p) Show that in case of A.C. the potential drop across an inductor lags the current by  $90^\circ$ . (2)

(q) A charged  $30\mu\text{F}$  capacitor is connected to a  $27\text{ mH}$  inductor. What is the frequency of free oscillations of the circuit? (3)

OR

**Q.4.(A)**

(x) Draw the frequency response curve for LCR parallel resonance. Give one application of a resonant circuit. (2)

(y) Draw a two port network and mention all the relevant z-parameters. (3)

**Q.4.(B)**

A D.C. source of e.m.f  $V$  volts is connected in series with a key, a capacitor of  $C$  Farads and a resistor of  $R\ \Omega$ . Find the maximum charge on the capacitor and the time taken for the charge to reach half its maximum value. (5)

**Q.5.(A)**

(p) How can the transformers be categorised as a step-up or step-down transformers? (2)

(q) A D.C. electromagnet is wound with 960 turns and has resistance of  $50\Omega$  when the exciting voltage is  $230\text{V}$ , the magnetic flux linking the coil is  $0.005\text{Wb}$ . Calculate the self – inductance of the coil and the energy stored in the magnetic field. (3)

OR

**Q.5.(A)**

(x) What is meant by an ideal transformer? Explain. (2)

(y) What is the self-inductance of a solenoid of length  $40\text{cm}$ , area of cross section  $20\text{cm}^2$  and total number of turns = 800? (3)

**Q.5.(B)**

Derive expression for average power supplied to resistance over a complete cycle in an A.C. circuit. (5)

**Q.6.(A)**

(p) Show that the capacitive reactance for pure capacitor circuit is infinite in case of D.C. supply. (2)

(q) Calculate the resonance frequency of an acceptor circuit with value of inductor and capacitor as  $20\text{mH}$  and  $5\mu\text{F}$  respectively. (3)

OR

**Q.6.(A)**

(x) Show that the inductive reactance for pure inductor circuit is zero in case of D.C. supply. (2)

(y) Calculate the resonance frequency of a rejector circuit with value of inductor and capacitor as  $60\text{mH}$  and  $25\mu\text{F}$  respectively. (3)

**Q.6.(B)**

Name the basic interconnection that can be done with two-port networks. Demonstrate at least two of them with neat circuit diagram. (5)