

**CARMEL COLLEGE OF ARTS, SCIENCE & COMMERCE FOR WOMEN,  
NUVEM-GOA  
SEMESTER END EXAMINATION, APRIL-MAY 2023**

**Semester:** IV of B.Sc

**Class:** S.Y.B.Sc

**Course Title & Code:** Electrical and Electronic Instrumentation PYS 105

**Maximum marks:** 60 **Date:** 23/05/2023 **Duration:** 2 Hours **Total No of pages:** 02

**Instructions:**


- 1) All questions are compulsory, however internal choice is available.
- 2) Figures to the right indicate maximum marks to the question.
- 3) Symbols have their usual meanings unless otherwise stated.
- 4) Draw neat diagram wherever necessary.
- 5) Use of non-programmable calculator is permitted.

**Q1. Answer any four of the following (4 x 2.5 = 10)**

- (A) Draw a labelled diagram of a PMMC instrument.
- (B) What is D'Arsonval movement?
- (C) What is a Watt hour meter? Mention the different types of watt-hour meter.
- (D) Explain how the problem of low sensitivity associated with electrodynamic meter for AC applications can be overcome?
- (E) What are AC and DC bridges?
- (F) Draw a labelled circuit diagram for Schering bridge.

**Q2. Answer any four of the following (4 x 2.5 = 10)**

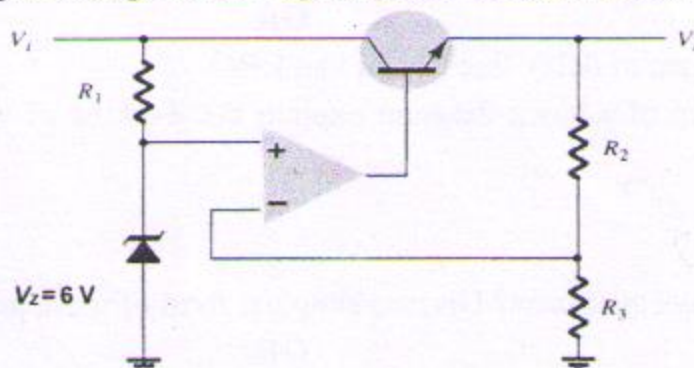- (A) Write the conditions that must be satisfied for the balance of AC bridges?
- (B) Draw the circuit diagram of bridge rectifier with LC filter.
- (C) Compute the output voltage for the Op-amp series regulator shown below:




In the above circuit  $V_i = 10V$ ,  $R_1 = 1k\Omega$ ,  $R_2 = 10k\Omega$ ,  $R_3 = 10k\Omega$

- (D) Draw the circuit diagram of sweep line generator.



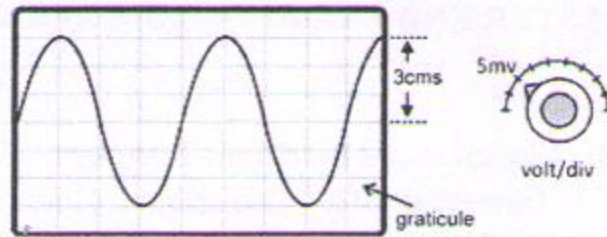- (E) Below figure shows the output of sine wave observed a CRO screen and the knob position of volt/div.



From the above figure, measure the peak to peak voltage of the signal.

- (F) Other than measurement of voltage of a sine wave signal, what other parameters of the same signal can be measured using CRO?

Q3.

- (A) How can a galvanometer be converted into a DC voltmeter? Explain. (5)

OR

- (B) Explain the working of disc type electrostatic voltmeter with the help of a diagram. (5)

- (C) Derive an expression for resistance using Kelvin's double bridge. (5)

Q4.

- (A) Explain the working of transistor shunt voltage regulator. (5)

OR

- (B) Explain the working of adjustable voltage regulator using LM 317. (5)

- (C) Draw the circuit diagram of step-down switching regulator and explain its working. (5)

Q5.

- (A) Draw the block diagram of CRO and briefly explain each component of the CRO. (5)

OR

- (B) Discuss the use of delay line circuit in a CRO. (5)

- (C) With the help of a block diagram explain the working of vertical amplifier in a CRO. (5)

Q6.

- (A) What are wave analyzers? Discuss simplest form of wave analyzers. (5)

OR

- (B) Discuss functioning of a digital multimeter with the help of a block diagram. (5)

- (C) Draw the block diagram of a standard AF sine-square wave generator and explain functioning of each block. (5)

\*\*\*\*\*